

# Homework #1

1. A machine with 4.2 GHz clock rate. What is its clock cycle time? \*

$$4.2 \text{ GHz} = 4.2 \times 10^9 \text{ sec} = 4200 \times 10^{-12} \text{ sec}$$


$$4.2 \text{ GHz} = 4200 \text{ picoseconds}$$

2. Program P has  $12 \times 10^9$  instructions. A 4 GHz machine has an average CPI of 2. What is the expected CPU time?

$$\begin{aligned} \text{CPU time} &= [\text{instruction count} \times \text{CPI}] / \text{clock rate} \\ &= [(12 \times 10^9) \times (2) \text{ cycles}] / 4 \times 10^9 \text{ cyc/sec} \\ &= \frac{24 \times 10^9 \text{ cyc} \cdot \text{sec}}{4 \times 10^9 \text{ cyc/sec}} \\ &= 6 \times 10^2 \text{ sec} \end{aligned}$$


$$\text{CPU time} = 600 \text{ seconds}$$

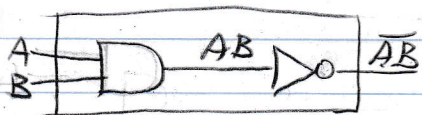3. Use a truth table to prove the two circuits are equivalent.




NAND

| A | B | $\overline{AB}$ |
|---|---|-----------------|
| 0 | 0 | 1               |
| 0 | 1 | 1               |
| 1 | 0 | 1               |
| 1 | 1 | 0               |

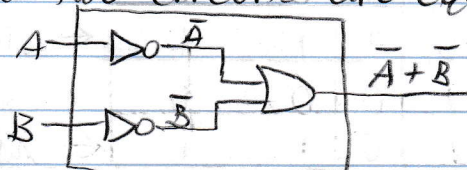

Negative OR

| A | B | $\overline{A} + \overline{B}$ |
|---|---|-------------------------------|
| 0 | 0 | 1                             |
| 0 | 1 | 1                             |
| 1 | 0 | 1                             |
| 1 | 1 | 0                             |

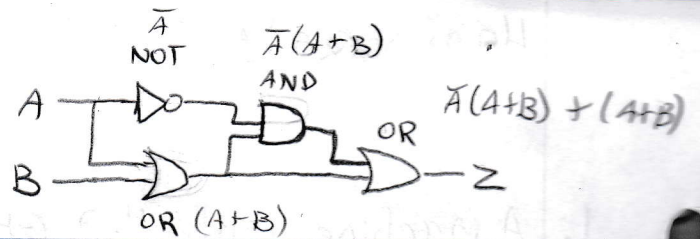

4. Given the logic circuit,  
a) write a logic equation for it.

$$Z = \bar{A}B + (A+B)$$

\*  $\bar{A}A = F$   
 $\bar{A}A + \bar{A}B = F + \bar{A}B$   
 \* This can be simplified  
 as  $Z = A + B$

- b) When  $A=1$  and  $B=0$ , what is  $Z$ ?

$$Z \text{ is true when } A=1 \text{ and } B=0$$

\*  $Z = (\bar{1})(0) + (1+0)$   
 $Z = 0 + 1$   
 $Z = 1$

5. Use 2-input AND, 2-input OR and inverter gates only to construct a circuit from the truth table.

| input |   |   | output |
|-------|---|---|--------|
| A     | B | C | X      |
| 0     | 0 | 0 | 1      |
| 0     | 0 | 1 | 0      |
| 0     | 1 | 0 | 0      |
| 0     | 1 | 1 | 1      |
| 1     | 0 | 0 | 0      |
| 1     | 0 | 1 | 1      |
| 1     | 1 | 0 | 1      |
| 1     | 1 | 1 | 0      |

$$X = (\bar{A}BC) + (A\bar{B}C) + (AB\bar{C}) + (\bar{A}\bar{B}C)$$

